 


# Working with combinational logic

- Simplification
  - two-level simplification
  - exploiting don't cares
  - algorithm for simplification
- Logic realization
  - two-level logic and canonical forms realized with NANDs and NORs
  - multi-level logic, converting between ANDs and ORs
- Time behavior
- Hardware description languages

# Design example: two-bit comparator



block diagram  
and  
truth table

A	B	C	D	LT	EQ	GT
0	0	0	0	0	1	0
		0	1	1	0	0
		1	0	1	0	0
		1	1	1	0	0
0	1	0	0	0	0	1
		0	1	0	1	0
		1	0	1	0	0
		1	1	1	0	0
1	0	0	0	0	0	1
		0	1	0	0	1
		1	0	0	1	0
		1	1	1	0	0
1	1	0	0	0	0	1
		0	1	0	0	1
		1	0	0	0	1
		1	1	0	1	0

we'll need a 4-variable Karnaugh map  
for each of the 3 output functions

# Design example: two-bit comparator (cont'd)

	A				
	0	0	0	0	
	1	0	0	0	D
C	1	1	0	1	
	1	1	0	0	
	B				

K-map for LT

	A				
	1	0	0	0	
	0	1	0	0	D
C	0	0	1	0	
	0	0	0	1	
	B				

K-map for EQ

	A				
	0	1	1	1	
	0	0	1	1	D
C	0	0	0	0	
	0	0	1	0	
	B				

K-map for GT


$$LT = A' B' D + A' C + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D' = (A \text{ xnor } C) \cdot (B \text{ xnor } D)$$


$$GT = B C' D' + A C' + A B D'$$

LT and GT are similar (flip A/C and B/D)
 
# Design example: two-bit comparator (cont'd)




 two alternative  
implementations of EQ  
with and without XOR



XNOR is implemented with  
at least 3 simple gates

# Design example: 2x2-bit multiplier




 


block diagram  
and  
truth table


A2	A1	B2	B1	P8	P4	P2	P1
0	0	0	0	0	0	0	0
		0	1	0	0	0	0
		1	0	0	0	0	0
		1	1	0	0	0	0
0	1	0	0	0	0	0	0
		0	1	0	0	0	1
		1	0	0	0	1	0
		1	1	0	0	1	1
1	0	0	0	0	0	0	0
		0	1	0	0	1	0
		1	0	0	1	0	0
		1	1	0	1	1	0
1	1	0	0	0	0	0	0
		0	1	0	0	1	1
		1	0	0	1	1	0
		1	1	1	0	0	1

4-variable K-map  
for each of the 4  
output functions
    
# Design example: 2x2-bit multiplier (cont'd)



# Design example: BCD increment by 1

 

block diagram  
and  
truth table

I8	I4	I2	I1	O8	O4	O2	O1
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

4-variable K-map for each of  
the 4 output functions

# Design example: BCD increment by 1 (cont'd)

			I8	
	0	0	X	1
	0	0	X	0
	0	1	X	X
	0	0	X	X
I2			I4	
				I1
				<u>O8</u>

$$O8 = I4 I2 I1 + I8 I1'$$

$$O4 = I4 I2' + I4 I1' + I4' I2 I1$$

$$O2 = I8' I2' I1 + I2 I1'$$

$$O1 = I1'$$

			I8	
	0	1	X	0
	0	1	X	0
	1	0	X	X
	0	1	X	X
I2			I4	
				I1
				<u>O4</u>

			I8	
	0	0	X	0
	1	1	X	0
	0	0	X	X
	1	1	X	X
I2			I4	
				I1
				<u>O2</u>

			I8	
	1	1	X	1
	0	0	X	0
	0	0	X	X
	1	1	X	X
I2			I4	
				I1
				<u>O1</u>



# Definition of terms for two-level simplification

- Implicant
  - single element of ON-set or DC-set or any group of these elements that can be combined to form a subcube
- Prime implicant
  - implicant that can't be combined with another to form a larger subcube
- Essential prime implicant
  - prime implicant is essential if it alone covers an element of ON-set
  - will participate in ALL possible covers of the ON-set
  - DC-set used to form prime implicants but not to make implicant essential
- Objective:
  - grow implicant into prime implicants (minimize literals per term)
  - cover the ON-set with as few prime implicants as possible (minimize number of product terms)

# Examples to illustrate terms

				A
	0	X	1	0
	1	1	1	0
C	1	0	1	1
	0	0	1	1
				B

6 prime implicants:

$A'B'D$ ,  $BC'$ ,  $AC$ ,  $A'C'D$ ,  $AB$ ,  $B'CD$

essential

minimum cover:  $AC + BC' + A'B'D$

5 prime implicants:

$BD$ ,  $ABC'$ ,  $ACD$ ,  $A'BC$ ,  $A'C'D$

essential

minimum cover: 4 essential implicants

				A
	0	0	1	0
	1	1	1	0
	0	1	1	1
C	0	1	0	0
				B

# Algorithm for two-level simplification

- Algorithm: minimum sum-of-products expression from a Karnaugh map
  - Step 1: choose an element of the ON-set
  - Step 2: find "maximal" groupings of 1s and Xs adjacent to that element
    - consider top/bottom row, left/right column, and corner adjacencies
    - this forms prime implicants (number of elements always a power of 2)
  - Repeat Steps 1 and 2 to find all prime implicants
  - Step 3: revisit the 1s in the K-map
    - if covered by single prime implicant, it is essential, and participates in final cover
    - 1s covered by essential prime implicant do not need to be revisited
  - Step 4: if there remain 1s not covered by essential prime implicants
    - select the smallest number of prime implicants that cover the remaining 1s

# Algorithm for two-level simplification (example)

	A				
	X	1	0	1	
	0	1	1	1	
C	0	X	X	0	D
	0	1	0	1	
	B				

	A				
	X	1	0	1	
	0	1	1	1	
C	0	X	X	0	D
	0	1	0	1	
	B				

2 primes around  $A'BC'D'$

	A				
	X	1	0	1	
	0	1	1	1	
C	0	X	X	0	D
	0	1	0	1	
	B				

2 primes around  $ABC'D$

	A				
	X	1	0	1	
	0	1	1	1	
C	0	X	X	0	D
	0	1	0	1	
	B				

3 primes around  $AB'C'D'$

	A				
	X	1	0	1	
	0	1	1	1	
C	0	X	X	0	D
	0	1	0	1	
	B				

2 essential primes

	A				
	X	1	0	1	
	0	1	1	1	
C	0	X	X	0	D
	0	1	0	1	
	B				

minimum cover (3 primes)

# Activity

- List all prime implicants for the following K-map:

A			
X	0	X	0
0	1	X	1
0	X	X	0
X	1	1	1
B			
C		D	

- Which are essential prime implicants?
- What is the minimum cover?