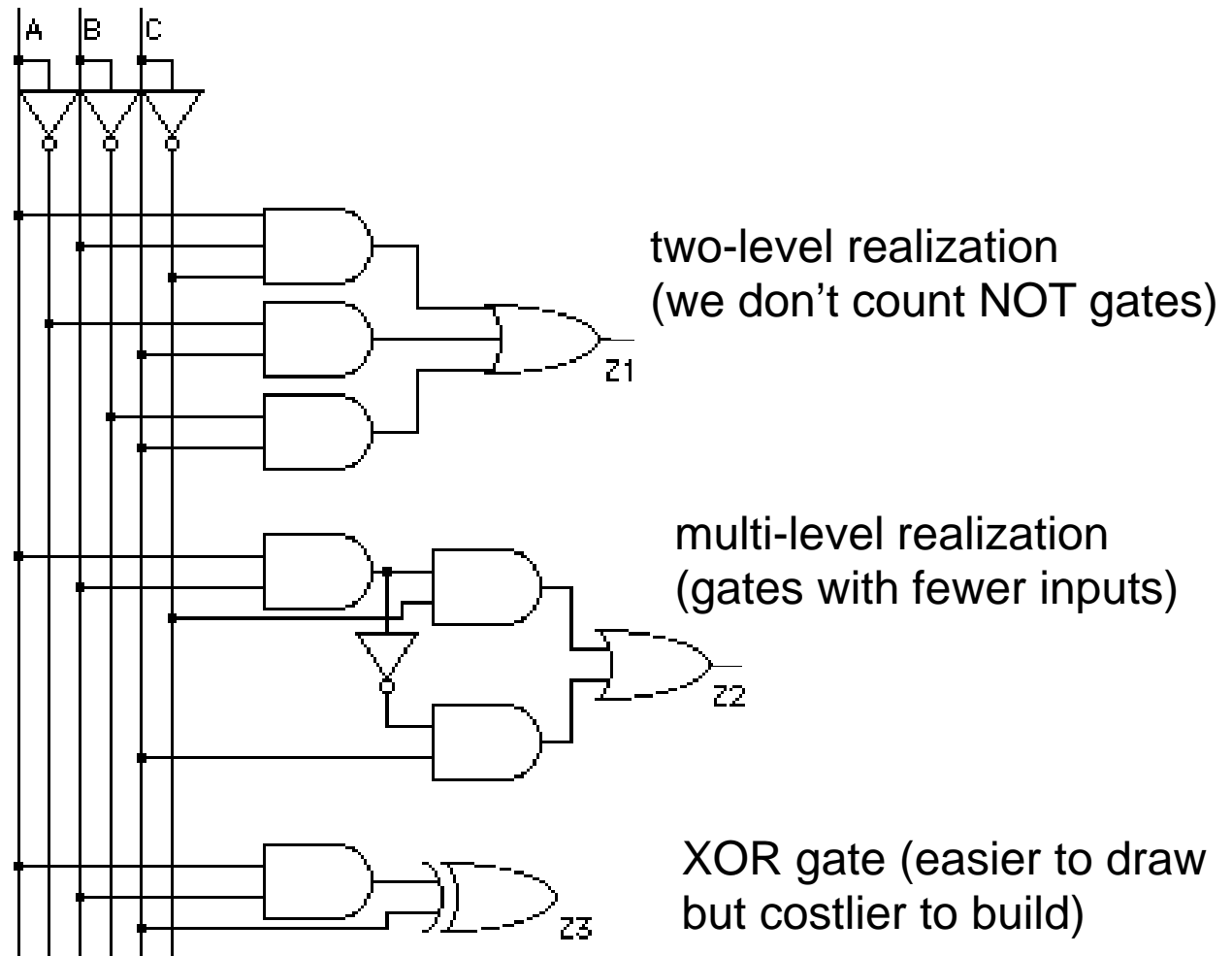


# Choosing different realizations of a function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0



# Which realization is best?


- Reduce number of inputs
  - literal: input variable (complemented or not)
    - can approximate cost of logic gate as 2 transistors per literal
    - why not count inverters?
  - fewer literals means less transistors
    - smaller circuits
  - fewer inputs implies faster gates
    - gates are smaller and thus also faster
  - fan-ins (# of gate inputs) are limited in some technologies
- Reduce number of gates
  - fewer gates (and the packages they come in) means smaller circuits
    - directly influences manufacturing costs

# Which is the best realization? (cont'd)

- Reduce number of levels of gates
  - fewer level of gates implies reduced signal propagation delays
  - minimum delay configuration typically requires more gates
    - wider, less deep circuits
- How do we explore tradeoffs between increased circuit delay and size?
  - automated tools to generate different solutions
  - logic minimization: reduce number of gates and complexity
  - logic optimization: reduction while trading off against delay
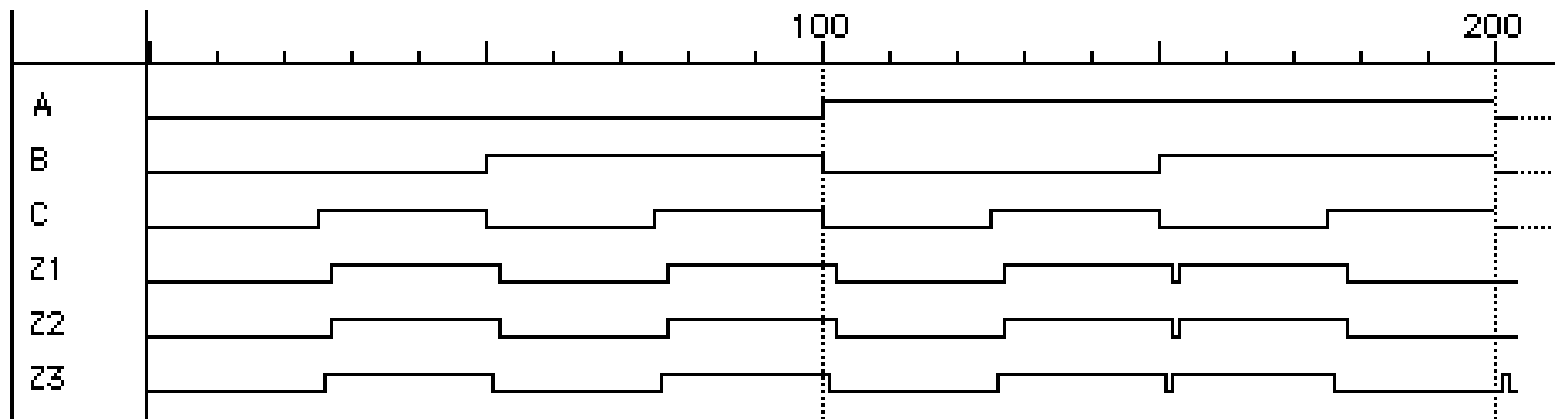
# Are all realizations equivalent?

- Under the same input stimuli, the three alternative implementations have almost the same waveform behavior
  - delays are different
  - glitches (hazards) may arise – these could be bad, it depends
  - variations due to differences in number of gate levels and structure
- The three implementations are functionally equivalent



# Implementing Boolean functions

- Technology independent
  - canonical forms
  - two-level forms
  - multi-level forms
- Technology choices
  - packages of a few gates
  - regular logic
  - two-level programmable logic
  - multi-level programmable logic

# Canonical forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
- Canonical forms
  - standard forms for a Boolean expression
  - provides a unique algebraic signature

# Sum-of-products canonical forms

- Also known as disjunctive normal form
- Also known as minterm expansion

			$F =$		$001$	$011$	$101$	$110$	$111$
			$F =$		$A'B'C$	$+ A'BC$	$+ AB'C$	$+ ABC'$	$+ ABC$
A	B	C	F	F'					
0	0	0	0	1					
0	0	1	1	0					
0	1	0	0	1					
0	1	1	1	0					
1	0	0	0	1					
1	0	1	1	0					
1	1	0	1	0					
1	1	1	1	0					


$F' = A'B'C' + A'BC' + AB'C'$

# Sum-of-products canonical form (cont'd)

- Product term (or minterm)
  - ANDed product of literals – input combination for which output is true
  - each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms	
0	0	0	$A'B'C'$	m0
0	0	1	$A'B'C$	m1
0	1	0	$A'BC'$	m2
0	1	1	$A'BC$	m3
1	0	0	$AB'C'$	m4
1	0	1	$AB'C$	m5
1	1	0	$ABC'$	m6
1	1	1	$ABC$	m7

short-hand notation for  
minterms of 3 variables



F in canonical form:

$$\begin{aligned}F(A, B, C) &= \Sigma m(1,3,5,6,7) \\&= m1 + m3 + m5 + m6 + m7 \\&= A'B'C + A'BC + AB'C + ABC' + ABC\end{aligned}$$

canonical form  $\neq$  minimal form

$$\begin{aligned}F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\&= (A'B' + A'B + AB' + AB)C + ABC' \\&= ((A' + A)(B' + B))C + ABC' \\&= C + ABC' \\&= ABC' + C \\&= AB + C\end{aligned}$$



# Product-of-sums canonical form

- Also known as conjunctive normal form
- Also known as maxterm expansion

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F =$        $000$                    $010$                    $100$   
 $F = (A + B + C) (A + B' + C) (A' + B + C)$


$$F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$$

# Product-of-sums canonical form (cont'd)

- Sum term (or maxterm)
  - ORed sum of literals – input combination for which output is false
  - each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7

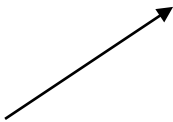short-hand notation for  
maxterms of 3 variables



F in canonical form:

$$\begin{aligned}F(A, B, C) &= \Pi M(0,2,4) \\&= M0 \cdot M2 \cdot M4 \\&= (A + B + C) (A + B' + C) (A' + B + C)\end{aligned}$$

canonical form  $\neq$  minimal form

$$\begin{aligned}F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\&= (A + B + C) (A + B' + C) \\&\quad (A + B + C) (A' + B + C) \\&= (A + C) (B + C)\end{aligned}$$

# S-o-P, P-o-S, and de Morgan's theorem

## ■ Sum-of-products

- $F' = A'B'C' + A'BC' + AB'C'$

## ■ Apply de Morgan's

- $(F')' = (A'B'C' + A'BC' + AB'C')'$

- $F = (A + B + C) (A + B' + C) (A' + B + C)$

## ■ Product-of-sums


- $F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$

## ■ Apply de Morgan's

- $(F')' = ( (A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C') )'$


- $F = A'B'C + A'BC + AB'C + ABC' + ABC$
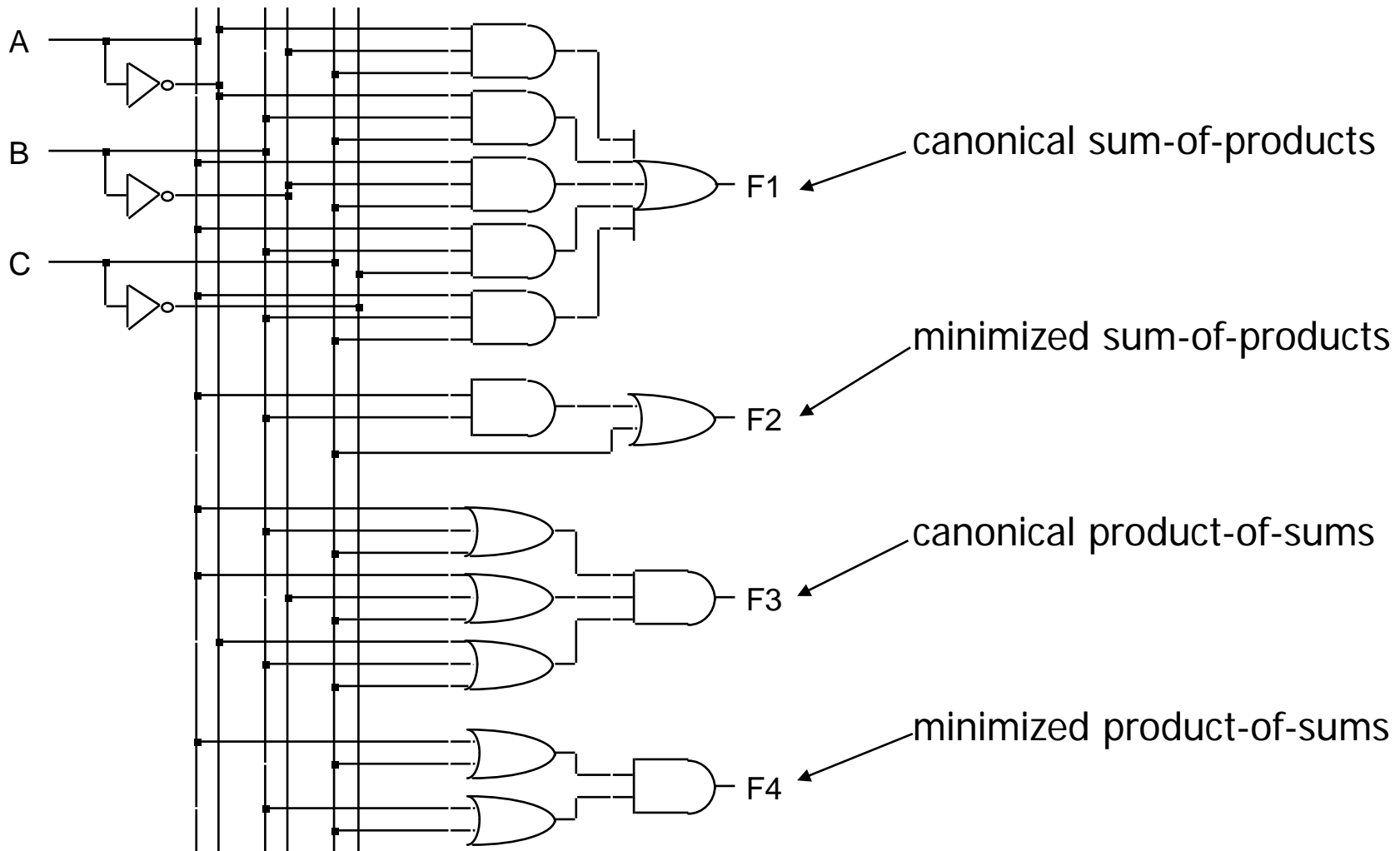
# Four alternative two-level implementations of $F = AB + C$


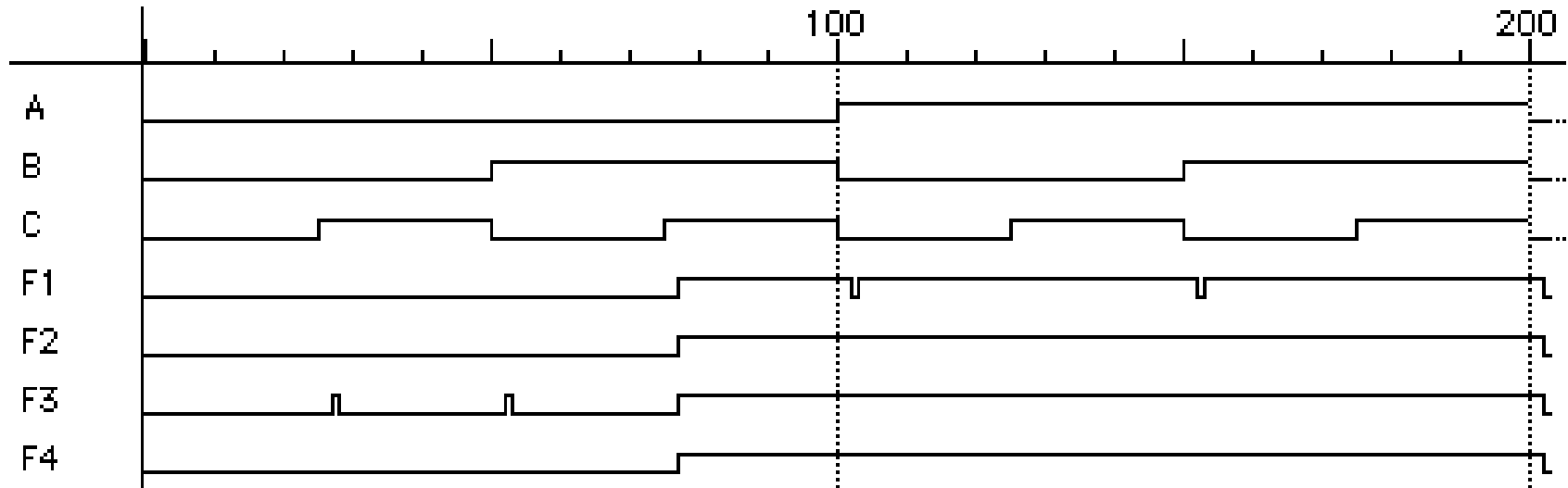
# Waveforms for the four alternatives

- Waveforms are essentially identical
  - except for timing hazards (glitches)
  - delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)



# Mapping between canonical forms

- Minterm to maxterm conversion
  - use maxterms whose indices do not appear in minterm expansion
  - e.g.,  $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm conversion
  - use minterms whose indices do not appear in maxterm expansion
  - e.g.,  $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm expansion of  $F$  to minterm expansion of  $F'$ 
  - use minterms whose indices do not appear
  - e.g.,  $F(A,B,C) = \sum m(1,3,5,6,7)$        $F'(A,B,C) = \sum m(0,2,4)$
- Maxterm expansion of  $F$  to maxterm expansion of  $F'$ 
  - use maxterms whose indices do not appear
  - e.g.,  $F(A,B,C) = \prod M(0,2,4)$        $F'(A,B,C) = \prod M(1,3,5,6,7)$

# Incompletely specified functions

- Example: binary coded decimal increment by 1
  - BCD digits encode the decimal digits 0 – 9 in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z	
0	0	0	0	0	0	0	1	
0	0	0	1	0	0	1	0	← off-set of W
0	0	1	0	0	0	1	1	
0	0	1	1	0	1	0	0	
0	1	0	0	0	1	0	1	← on-set of W
0	1	0	1	0	1	1	0	
0	1	1	0	0	1	1	1	← don't care (DC) set of W
0	1	1	1	1	0	0	0	
1	0	0	0	1	0	0	1	
1	0	0	1	0	0	0	0	←
1	0	1	0	X	X	X	X	
1	0	1	1	X	X	X	X	
1	1	0	0	X	X	X	X	
1	1	0	1	X	X	X	X	
1	1	1	0	X	X	X	X	
1	1	1	1	X	X	X	X	

these inputs patterns should never be encountered in practice – **"don't care"** about associated output values, can be exploited in minimization

# Notation for incompletely specified functions

- Don't cares and canonical forms
  - so far, only represented on-set
  - also represent don't-care-set
  - need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
  - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
  - $Z = \Sigma [ m(0,2,4,6,8) + d(10,11,12,13,14,15) ]$
  - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
  - $Z = \Pi [ M(1,3,5,7,9) \cdot D(10,11,12,13,14,15) ]$



# Simplification of two-level combinational logic

- Finding a minimal sum of products or product of sums realization
  - exploit don't care information in the process
- Algebraic simplification
  - not an algorithmic/systematic procedure
  - how do you know when the minimum realization has been found?
- Computer-aided design tools
  - precise solutions require very long computation times, especially for functions with many inputs ( $> 10$ )
  - heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
  - to understand automatic tools and their strengths and weaknesses
  - ability to check results (on small examples)

# The uniting theorem

- Key tool to simplification:  $A(B' + B) = A$
- Essence of simplification of two-level logic
  - find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$





A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

B has the same value in both on-set rows  
– B remains

A has a different value in the two rows  
– A is eliminated
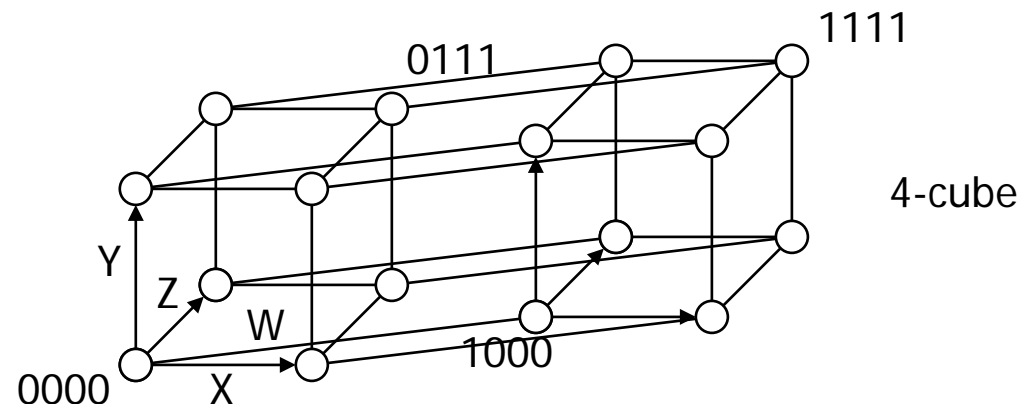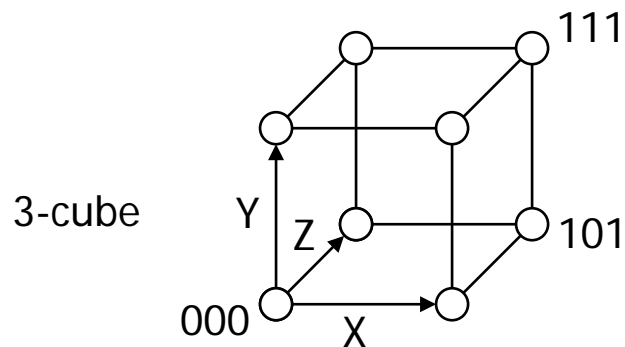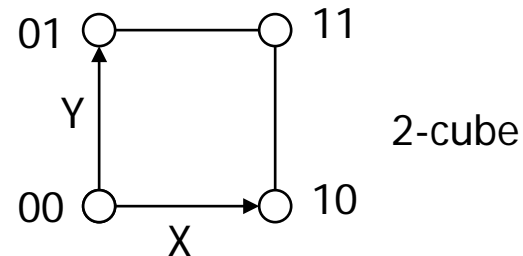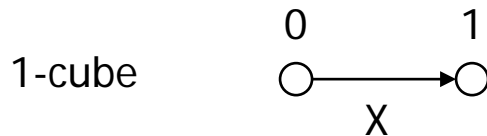
# Boolean cubes


- Visual technique for indentifying when the uniting theorem can be applied
- $n$  input variables =  $n$ -dimensional "cube"



# Mapping truth tables onto Boolean cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

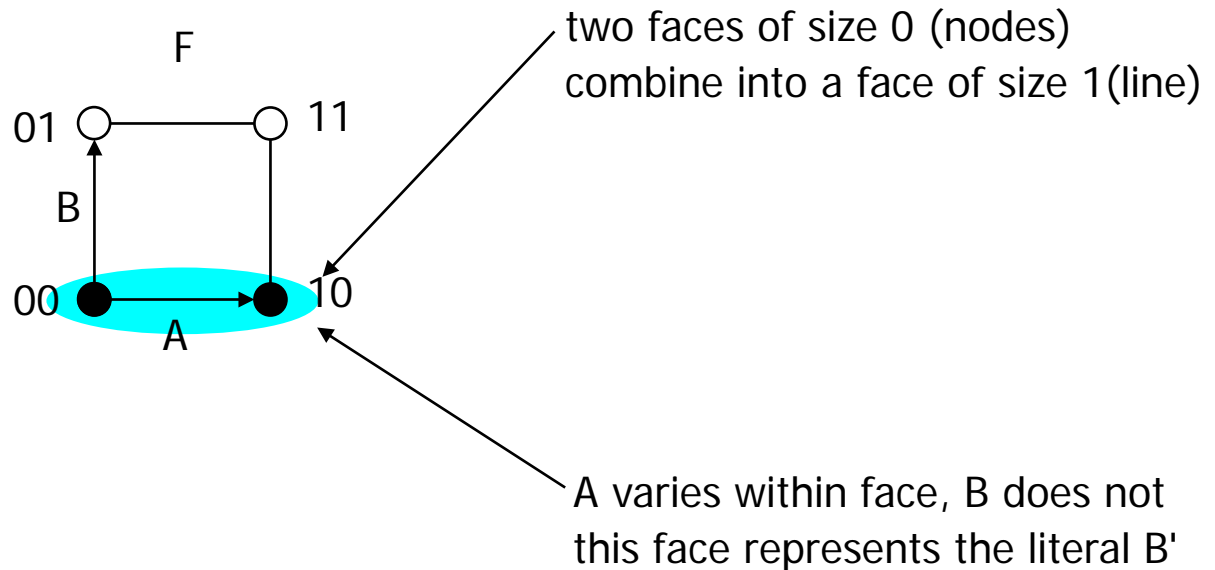


ON-set = solid nodes  
OFF-set = empty nodes  
DC-set = x'd nodes

# Three variable example

## ■ Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

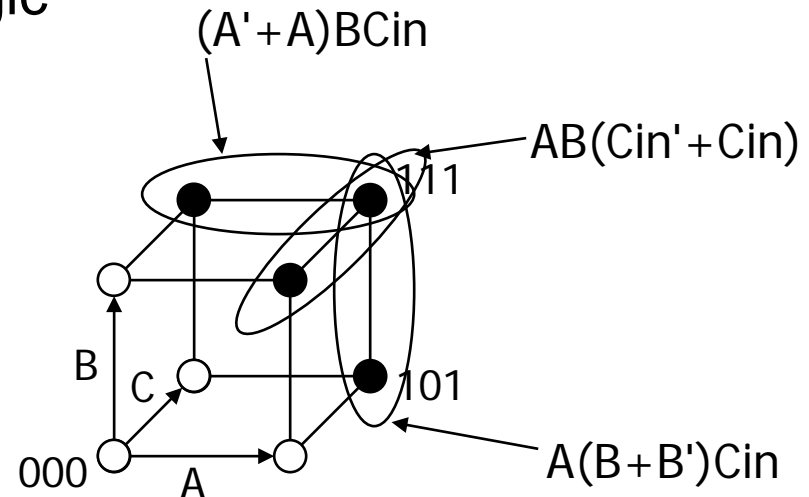


the on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$\text{Cout} = \text{BCin} + \text{AB} + \text{ACin}$$

# Higher dimensional cubes

- Sub-cubes of higher dimension than 2

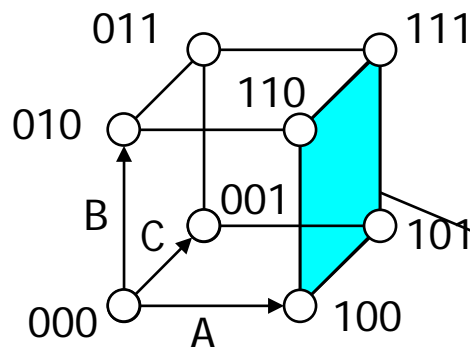

$$F(A,B,C) = \Sigma m(4,5,6,7)$$

on-set forms a square  
i.e., a cube of dimension 2

*represents an expression in one variable  
i.e., 3 dimensions – 2 dimensions*

A is asserted (true) and unchanged  
B and C vary

This subcube represents the  
literal A

# m-dimensional cubes in a n-dimensional Boolean space

- In a 3-cube (three variables):
  - a 0-cube, i.e., a single node, yields a term in 3 literals
  - a 1-cube, i.e., a line of two nodes, yields a term in 2 literals
  - a 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
  - a 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
  - an m-subcube within an n-cube ( $m < n$ ) yields a term with  $n - m$  literals

# Karnaugh maps

- Flat map of Boolean cube
  - wrap-around at edges
  - hard to draw and visualize for more than 4 dimensions
  - virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
  - guide to applying the uniting theorem
  - on-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

		A	
		0	1
B	0	1 0	1 2
	1	0 1	0 3

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0



# Karnaugh maps (cont'd)

- Numbering scheme based on Gray-code
  - e.g., 00, 01, 11, 10
  - only a single bit changes in code for adjacent map cells

AB		A			
		00	01	11	10
C	0	0	2	6	4
	1	1	3	7	5

B

		A			
		0	2	6	4
C	0	0	2	6	4
	1	1	3	7	5

B



		A			
		0	4	12	8
C	0	0	4	12	8
	1	1	5	13	9
C	2	3	7	15	11
	3	2	6	14	10

B

$$13 = 1101 = ABC'D$$
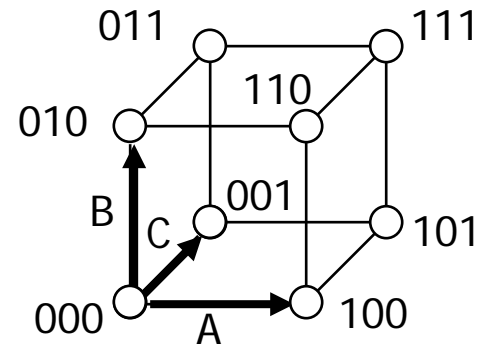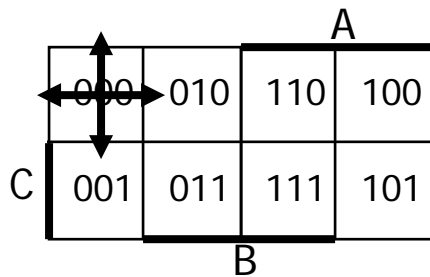
# Adjacencies in Karnaugh maps

- Wrap from first to last column
- Wrap top row to bottom row



# Karnaugh map examples

■  $F =$

	A	
B	0	1
	1	1
B'	0	1
	0	0

■  $C_{out} =$

	A			
Cin	0	0	1	0
	0	1	1	1
B	0	1	0	1
	0	1	1	1

$B'$

$AB + AC_{in} + BC_{in}$

■  $f(A,B,C) = \Sigma m(0,4,5,7)$

	A			
C	0	0	1	0
	1	0	0	1
B	0	1	0	1
	0	0	1	1

$AC + B'C' + AB'$

obtain the complement of the function by covering 0s with subcubes

# More Karnaugh map examples

			A
	0	0	1
	0	0	1
C	0	0	1
		B	

$$G(A,B,C) = A$$

			A
	1	0	0
	1	0	1
C	0	0	1
		B	

$$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$$

			A
	0	1	1
	1	1	0
C	1	1	0
		B	



F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$$

# Karnaugh map: 4-variable example

■  $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$

$$F = C + A'BD + B'D'$$

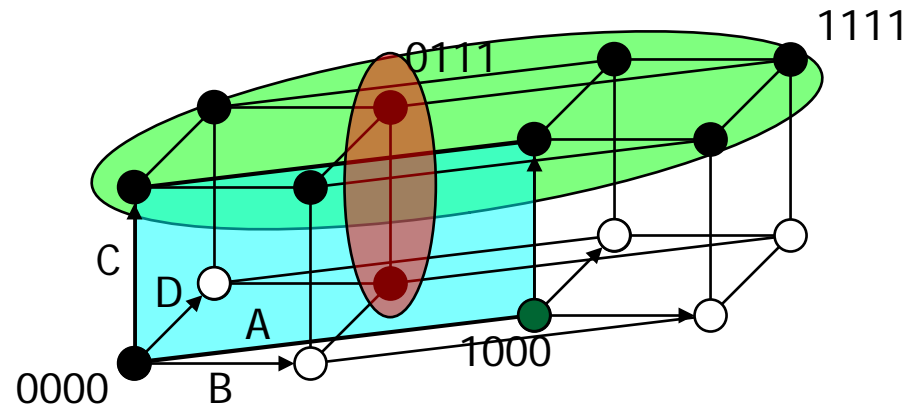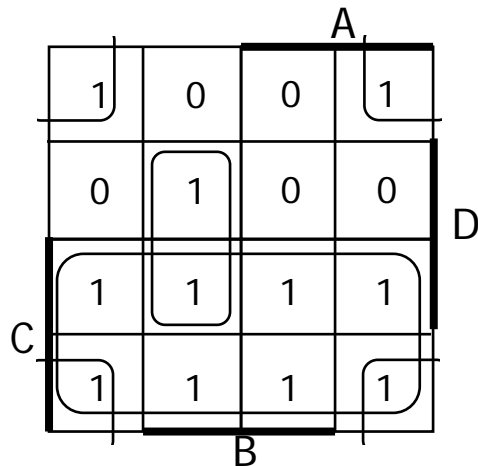

find the smallest number of the largest possible subcubes to cover the ON-set  
(fewer terms with fewer inputs per term)

# Karnaugh maps: don't cares

- $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$ 
  - without don't cares
    - $f = A'D + B'C'D$

A			
0	0	X	0
1	1	X	1
1	1	0	0
0	X	0	0
B			
C			
D			

# Karnaugh maps: don't cares (cont'd)

■  $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$

□  $f = A'D + B'C'D$

without don't cares

□  $f = A'D + C'D$

with don't cares

		A		
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
		B		

by using don't care as a "1"  
a 2-cube can be formed  
rather than a 1-cube to cover  
this node

don't cares can be treated as  
1s or 0s  
depending on which is more  
advantageous

# Activity

- Minimize the function  $F = \Sigma m(0, 2, 7, 8, 14, 15) + d(3, 6, 9, 12, 13)$



# Combinational logic summary

- Logic functions, truth tables, and switches
  - NOT, AND, OR, NAND, NOR, XOR, . . ., minimal set
- Axioms and theorems of Boolean algebra
  - proofs by re-writing and perfect induction
- Gate logic
  - networks of Boolean functions and their time behavior
- Canonical forms
  - two-level and incompletely specified functions
- Simplification
  - a start at understanding two-level simplification
- Later
  - automation of simplification
  - multi-level logic
  - time behavior
  - hardware description languages
  - design case studies