

Combinational logic

- Basic logic
 - Boolean algebra, proofs by re-writing, proofs by perfect induction
 - logic functions, truth tables, and switches
 - NOT, AND, OR, NAND, NOR, XOR, . . . , minimal set
- Logic realization
 - two-level logic and canonical forms
 - incompletely specified functions
- Simplification
 - uniting theorem
 - grouping of terms in Boolean functions
- Alternate representations of Boolean functions
 - cubes
 - Karnaugh maps

Possible logic functions of two variables

- There are 16 possible functions of 2 input variables:
 - in general, there are $2^{(2^n)}$ functions of n inputs



X	Y	16 possible functions (F0–F15)															
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		0		X		Y		X <u>xor</u> Y		X <u>or</u> Y		X <u>nor</u> Y not (X <u>or</u> Y)		X = Y		not Y	
		X <u>and</u> Y												not X		X <u>nand</u> Y not (X <u>and</u> Y)	

Cost of different logic functions

- Different functions are easier or harder to implement
 - each has a cost associated with the number of switches needed
 - 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
 - X (F3) and Y (F5): require 0 switches, output is one of inputs
 - X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
 - X nor Y (F4) and X nand Y (F14): require 4 switches
 - X or Y (F7) and X and Y (F1): require 6 switches
 - $X = Y$ (F9) and $X \oplus Y$ (F6): require 16 switches
- thus, because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice

Minimal set of functions

- Can we implement all logic functions from NOT, NOR, and NAND?
 - For example, implementing X and Y is the same as implementing $\text{not } (X \text{ nand } Y)$
- In fact, we can do it with only NOR or only NAND
 - NOT is just a NAND or a NOR with both inputs tied together

X	Y	X nor Y
0	0	1
1	1	0

X	Y	X nand Y
0	0	1
1	1	0

- and NAND and NOR are "duals", that is, its easy to implement one using the other

$$\begin{aligned} X \text{ nand } Y &\equiv \text{not } ((\text{not } X) \text{ nor } (\text{not } Y)) \\ X \text{ nor } Y &\equiv \text{not } ((\text{not } X) \text{ nand } (\text{not } Y)) \end{aligned}$$

- But lets not move too fast . . .
 - lets look at the mathematical foundation of logic

An algebraic structure

■ An algebraic structure consists of

- a set of elements B
- binary operations $\{ + , \bullet \}$
- and a unary operation $\{ ' \}$
- such that the following axioms hold:

1. the set B contains at least two elements: a, b

2. closure: $a + b$ is in B

$a \bullet b$ is in B

3. commutativity: $a + b = b + a$

$a \bullet b = b \bullet a$

4. associativity: $a + (b + c) = (a + b) + c$

$a \bullet (b \bullet c) = (a \bullet b) \bullet c$

5. identity: $a + 0 = a$

$a \bullet 1 = a$

6. distributivity: $a + (b \bullet c) = (a + b) \bullet (a + c)$

$a \bullet (b + c) = (a \bullet b) + (a \bullet c)$

7. complementarity: $a + a' = 1$

$a \bullet a' = 0$

Boolean algebra

- Boolean algebra
 - $B = \{0, 1\}$
 - variables
 - $+$ is logical OR, \bullet is logical AND
 - $'$ is logical NOT
- All algebraic axioms hold

Logic functions and Boolean algebra

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: ', +, and •

X	Y	$X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X'	$X' \cdot Y$
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

X	Y	X'	Y'	$X \cdot Y$	$X' \cdot Y'$	$(X \cdot Y) + (X' \cdot Y')$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \cdot Y) + (X' \cdot Y') \equiv X = Y$$

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

X, Y are Boolean algebra variables

Axioms and theorems of Boolean algebra

- identity

- 1. $X + 0 = X$

- 1D. $X \cdot 1 = X$

- null

- 2. $X + 1 = 1$

- 2D. $X \cdot 0 = 0$

- idempotency:

- 3. $X + X = X$

- 3D. $X \cdot X = X$

- involution:

- 4. $(X')' = X$

- complementarity:

- 5. $X + X' = 1$

- 5D. $X \cdot X' = 0$

- commutativity:

- 6. $X + Y = Y + X$

- 6D. $X \cdot Y = Y \cdot X$

- associativity:

- 7. $(X + Y) + Z = X + (Y + Z)$

- 7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$

Axioms and theorems of Boolean algebra (cont'd)

- distributivity:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z) \quad 8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

- uniting:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

- absorption:

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

- factoring:

$$12. (X + Y) \cdot (X' + Z) = \\ X \cdot Z + X' \cdot Y$$

$$12D. X \cdot Y + X' \cdot Z = \\ (X + Z) \cdot (X' + Y)$$

- consensus:

$$13. (X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = \\ X \cdot Y + X' \cdot Z$$

$$13D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) = \\ (X + Y) \cdot (X' + Z)$$

Axioms and theorems of Boolean algebra (cont'd)

- de Morgan's:

$$14. (X + Y + \dots)' = X' \cdot Y' \cdot \dots \quad 14D. (X \cdot Y \cdot \dots)' = X' + Y' + \dots$$

- generalized de Morgan's:

$$15. f'(X_1, X_2, \dots, X_n, 0, 1, +, \bullet) = f(X_1', X_2', \dots, X_n', 1, 0, \bullet, +)$$

- establishes relationship between \bullet and $+$

Axioms and theorems of Boolean algebra (cont'd)

■ Duality

- a dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
- any theorem that can be proven is thus also proven for its dual!
- a meta-theorem (a theorem about theorems)

■ duality:

$$16. X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$$

■ generalized duality:

$$17. f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

■ Different than deMorgan's Law

- this is a statement about theorems
- this is not a way to manipulate (re-write) expressions

Proving theorems (rewriting)

■ Using the axioms of Boolean algebra:

□ e.g., prove the theorem: $X \cdot Y + X \cdot Y' = X$

distributivity (8)	$X \cdot Y + X \cdot Y'$	$=$	$X \cdot (Y + Y')$
complementarity (5)	$X \cdot (Y + Y')$	$=$	$X \cdot (1)$
identity (1D)	$X \cdot (1)$	$=$	$X \checkmark$

□ e.g., prove the theorem: $X + X \cdot Y = X$

identity (1D)	$X + X \cdot Y$	$=$	$X \cdot 1 + X \cdot Y$
distributivity (8)	$X \cdot 1 + X \cdot Y$	$=$	$X \cdot (1 + Y)$
identity (2)	$X \cdot (1 + Y)$	$=$	$X \cdot (1)$
identity (1D)	$X \cdot (1)$	$=$	$X \checkmark$

Activity

- Prove the following using the laws of Boolean algebra:
 - $(X \cdot Y) + (Y \cdot Z) + (X' \cdot Z) = X \cdot Y + X' \cdot Z$

Proving theorems (perfect induction)

- Using perfect induction (complete truth table):
 - e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented


X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

A simple example: 1-bit binary adder

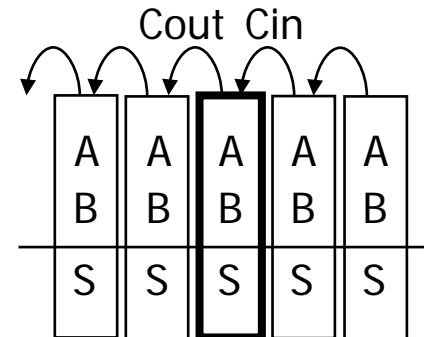- Inputs: A, B, Carry-in
- Outputs: Sum, Carry-out



A	B	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$S = A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin}$$

$$\text{Cout} = A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin}$$

Apply the theorems to simplify expressions

- The theorems of Boolean algebra can simplify Boolean expressions
 - e.g., full adder's carry-out function (same rules apply to any function)

$$\begin{aligned}\text{Cout} &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\ &= A' B \text{Cin} + A B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (A' + A) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= (1) B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + \boxed{A B \text{Cin} + A B \text{Cin}} \\ &= B \text{Cin} + A B' \text{Cin} + A B \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (B' + B) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A (1) \text{Cin} + A B \text{Cin}' + A B \text{Cin} \\ &= B \text{Cin} + A \text{Cin} + A B (\text{Cin}' + \text{Cin}) \\ &= B \text{Cin} + A \text{Cin} + A B (1) \\ &= B \text{Cin} + A \text{Cin} + A B\end{aligned}$$

adding extra terms
creates new factoring
opportunities

Activity

- Fill in the truth-table for a circuit that checks that a 4-bit number is divisible by 2, 3, or 5


X8	X4	X2	X1	By2	By3	By5
0	0	0	0	1	1	1
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	0	1	1	0	1	0

- Write down Boolean expressions for By2, By3, and By5

Activity

From Boolean expressions to logic gates

■ NOT X' \bar{X} $\sim X$

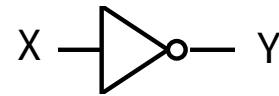


X	Y
0	1
1	0

■ AND $X \cdot Y$ XY $X \wedge Y$



X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

■ OR $X + Y$ $X \vee Y$

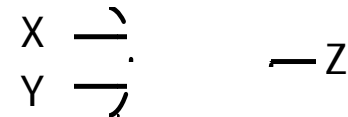

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

From Boolean expressions to logic gates (cont'd)

■ NAND




X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

■ NOR



X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


■ XOR $X \oplus Y$

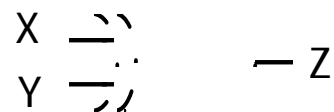

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$X \text{ xor } Y = X Y' + X' Y$
X or Y but not both
("inequality", "difference")

■ XNOR $X = Y$

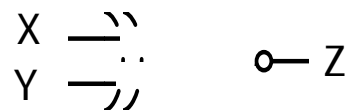



X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$X \text{ xnor } Y = X Y + X' Y'$
X and Y are the same
("equality", "coincidence")

From Boolean expressions to logic gates (cont'd)


- More than one way to map expressions to gates

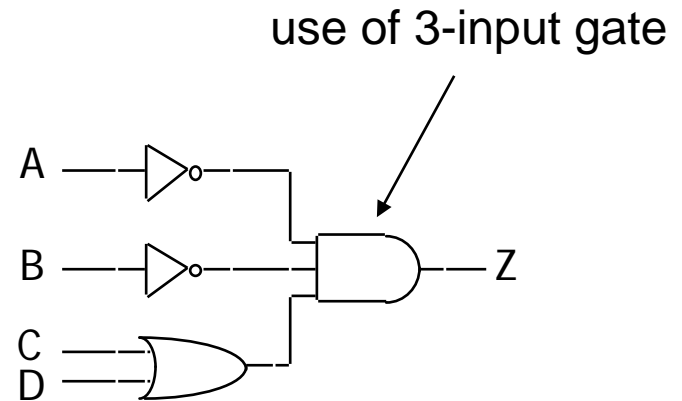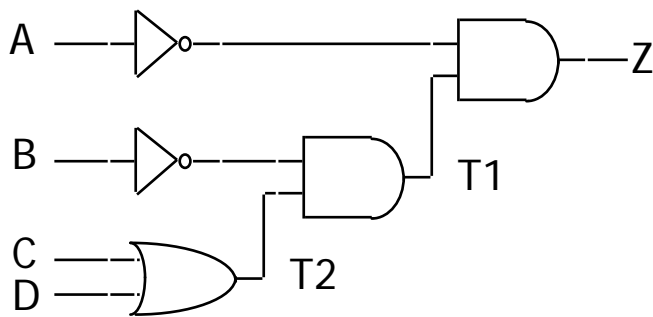□ e.g., $Z = A' \cdot B' \cdot (C + D) = (A' \cdot \underbrace{(B' \cdot (C + D))}_{T2})_{T1}$



Waveform view of logic functions

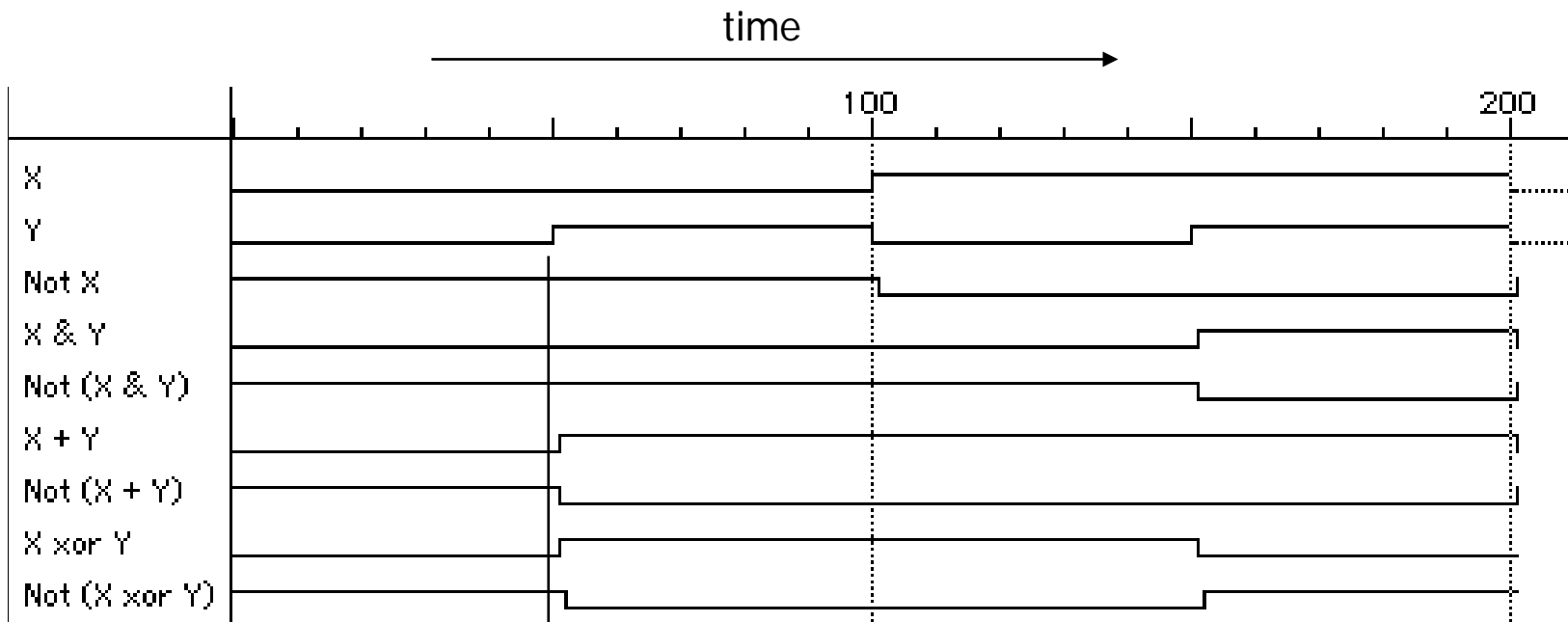- Just a sideways truth table
 - but note how edges don't line up exactly
 - it takes time for a gate to switch its output!



change in Y takes time to "propagate" through gates