

# Realizing Circuits with Different Kinds of FFs

## *Choosing a Flipflop*

### R-S Clocked Latch:

- used as storage element in narrow width clocked systems
- its use is not recommended!
- however, fundamental building block of other flipflop types

### J-K Flipflop:

- versatile building block
- can be used to implement D and T FFs
- usually requires least amount of logic to implement  $f(\text{In}, Q, Q+)$
- but has two inputs with increased wiring complexity

- because of 1's catching, never use master/slave J-K FFs
- edge-triggered varieties exist

### D Flipflop:

- minimizes wires, much preferred in VLSI technologies
- simplest design technique
- best choice for storage registers

### T Flipflops:

- don't really exist, constructed from J-K FFs
- usually best choice for implementing counters

Preset and Clear inputs highly desirable!!

# Realizing Circuits with Different Kinds of FFs

## Characteristic Equations:

R-S:  $Q+ = S + \bar{R} Q$

D:  $Q+ = D$


J-K:  $Q+ = J \bar{Q} + \bar{K} Q$

T:  $Q+ = T \bar{Q} + \bar{T} Q$


Derived from the K-maps  
for  $Q+ = f(\text{Inputs}, Q)$

E.g.,  $J=K=0$ , then  $Q+ = Q$   
 $J=1, K=0$ , then  $Q+ = 1$   
 $J=0, K=1$ , then  $Q+ = 0$   
 $J=1, K=1$ , then  $Q+ = \bar{Q}$
 
## Implementing One FF in Terms of Another



D implemented with J-K

 

J-K implemented with D

# Activity

*Characteristic Equations:*

$$\text{R-S: } Q^+ = S + \overline{R} Q$$

$$\text{D: } Q^+ = D$$

$$\text{J-K: } Q^+ = J \overline{Q} + \overline{K} Q$$

$$\text{T: } Q^+ = T \overline{Q} + \overline{T} Q$$

- Excitation Tables: What are the necessary inputs to cause a particular kind of change in state?

Q	Q <sup>+</sup>	R	S	J	K	T	D
0	0						
0	1						
1	0						
1	1						

# Realizing Circuits with Different Kinds of FFs

## Design Procedure

Excitation Tables: What are the necessary inputs to cause a particular kind of change in state?

Q	Q <sup>+</sup>	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

Implementing D FF with a J-K FF:

- 1) Start with K-map of  $Q^+ = f(D, Q)$
- 2) Create K-maps for J and K with same inputs (D, Q)
- 3) Fill in K-maps with appropriate values for J and K to cause the same state changes as in the original K-map

		D	
		0	1
Q	0	0	1
	1	0	1

$Q^+ = D$

E.g.,  $D = Q = 0$ ,  $Q^+ = 0$   
then  $J = 0$ ,  $K = X$

		D	
		0	1
Q	0	0	1
	1	X	X

$J = D$

		D	
		0	1
Q	0	X	X
	1	1	0

$K = \bar{D}$

# Realizing Circuits with Different Kinds of FFs

## Design Procedure (Continued)

Implementing J-K FF with a D FF:

1) K-Map of  $Q^+ = F(J, K, Q)$

2,3) Revised K-map using D's excitation table

its the same! that is why design procedure with D FF is simple!

		JK			
		J			
Q		00	01	11	10
	0	0	0	1	1
	1	1	0	0	1
		K			

$$Q^+ = D = J\bar{Q} + \bar{K}Q$$

Resulting equation is the combinational logic input to D to cause same behavior as J-K FF. Of course it is identical to the characteristic equation for a J-K FF.