

Curso: Bacharelado em Ciência da Computação
Disciplina: Introdução aos Sistemas Lógicos
2o. Semestre de 2017
Professor: Luiz Filipe Menezes Vieira (lfvieira@dcc.ufmg.br)

Data da entrega: 25.09.2017

Lista de Exercícios 2

Exercícios Teóricos

1. Consider the function $f(A, B, C, D) = \sum m(0, 1, 2, 7, 8, 9, 10, 15)$.
 - (a) Write this as a Boolean expression in canonical minterm form.
 - (b) Rewrite the expression in canonical maxterm form.
 - (c) Write the complement of f in “little m ” notation and as a canonical minterm expression.
 - (d) Write the complement of f in “big M ” notation and as a canonical maxterm expression.
2. Given the following function in product of sums form, not necessarily minimized:
 $F(W, X, Y, Z) = (W + \bar{X} + \bar{Y})(\bar{W} + \bar{Z})(W + Y)$
 - (a) Express the function in the canonical sum of products form. Use “little m ” notation.
 - (b) Reexpress the function in minimized sum of products form.
 - (c) Express \bar{F} in minimized sum of products form.
 - (d) Reexpress \bar{F} in minimized product of sums form.
3. Use Karnaugh maps (K-maps) to simplify the following functions in sum of products form. How many literals appear in your minimized solutions?
 - (b) $f(W, X, Y, Z) = \prod M(1, 3, 7, 9, 11, 15)$
 - (c) $f(A, B, C, D) = \sum m(0, 1, 4, 5, 12, 13)$
4. Determine the minimized realization of the following function in the sum of products form:
 $f(W, X, Y, Z) = \sum m(1, 7, 11, 13) + \sum d(0, 5, 10, 15)$
5. Show the following:
 - (a) A positive logic AND is equivalent to a negative logic OR.
 - (b) A positive logic NOR is equivalent to a negative logic NAND.
 - (c) A positive logic XOR is equivalent to a negative logic XNOR.
 - (d) A positive logic XNOR is equivalent to a negative logic XOR.

6. Consider a five-input Boolean function that is asserted whenever exactly two of its inputs are asserted.
 - (a) Construct its truth table.
 - (b) What is the function in sum of products form, using “little m ” notation?
 - (c) What is the function in product of sums form, using “big M ” notation?
 - (d) Use the Karnaugh map method to simplify the function in sum of products form.
7. Design a combinational circuit with three data inputs D_2, D_1, D_0 , two control inputs C_1, C_0 , and two outputs R_1, R_0 . R_1 and R_0 should be the remainder after dividing the binary number formed from D_2, D_1, D_0 by the number formed by C_1, C_0 . For example, if $D_2, D_1, D_0 = 111$ and $C_1, C_0 = 10$, then $R_1, R_0 = 01$ (that is, the remainder of 7 divided by 2 is 1). Note that division by zero will never be requested.
 - (a) Fill in truth tables for the combinational logic functions R_1 and R_0 .
 - (b) Derive minimized sum of product realizations of these functions using the Karnaugh map method.
 - (c) Draw a circuit schematic that implements R_1 and R_0 using NAND gates only. You may assume any fan-in gates that you need.
8. Given the following function in sum of products form (not necessarily minimized):
 $F(A, B, C, D) = \overline{A}BC + AD + AC$. Reexpress the function in:
 - (a) Canonical product of sums form. Use $\prod M$ notation.
 - (b) Minimized product of sums form.
 - (c) \overline{F} in minimized product of sums form.
 - (d) \overline{F} in minimized sum of product form.
 - (e) Implement F and \overline{F} using NAND gates only. You may assume that literals and their complements are available.
9. Factor the following sum of products expressions:
 - (a) $ABCD + ABDE$
 - (c) $AC + ADE + BC + BDE$
10. Given the following specification of Boolean functions, implement them in a hazard-free manner:
 - (a) $F(A, B, C) = B\overline{C} + \overline{A}C$
 - (d) $F(A, B, C, D) = \prod M(0, 1, 3, 5, 7, 8, 9, 13, 15)$
11. Implement the function $f(A, B, C, D, E) = A + \overline{C}D + B\overline{D} + \overline{B}D + \overline{B}CE$ using a multiplexer and no other logic. The constants logic 1, logic 0, and the variables, but not their complements, are available.
12. The truth table for a 1-bit combinational binary subtractor, analogous to the half adder, computing $D(\text{ifference}) = A \text{ minus } B$, with BL (borrow-from-left), is

| A | B | D | BL |
|---|---|---|----|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

- (a) Design a 1-bit combinational binary subtractor, comparable to the full adder, with two data inputs (A , B), a borrow from the right input (BI), a borrow request to the left output (BL), and a difference output (D).
- (b) Show how your design can be cascaded to form multibit-subtractors.
- (c) Does the subtractor work correctly for negative two's complement numbers?
- (d) How is a subtraction underflow condition indicated?
13. Implement to the gate level an ALU bit slice with three operation selection inputs, S_2 , S_1 , S_0 , that implements the following eight functions of the two data inputs A and B (and carry-in C_n):

| S_2 | S_1 | S_0 | ALU operation |
|-------|-------|-------|---------------------|
| 0 | 0 | 0 | $F_i = 0$ |
| 0 | 0 | 1 | $F_i = B$ minus A |
| 0 | 1 | 0 | $F_i = A$ minus B |
| 0 | 1 | 1 | $F_i = A$ plus B |
| 1 | 0 | 0 | $F_i = A$ XOR B |
| 1 | 0 | 1 | $F_i = A$ OR B |
| 1 | 1 | 0 | $F_i = A$ AND B |
| 1 | 1 | 1 | $F_i = 1$ |

Assume a simple ripple carry scheme between bit slices.

14. [Katz Capítulo 4, Exercício 4.24] (Word Problems)
 You are to design a converter that maps a 4-bit binary code into a 4-bit Gray code. The 4-bit Gray code sequence is defined as follows: 0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000. Give the truth table, and show how to implement this code converter as a ROM circuit and as a PLA circuit.